

Integrated Circuit Design

Homework #2

Due: 2019/03/27 13:00

1. Setup HSPICE following the steps listed in [20190313_T2_Hspice.pdf](#).
2. Use [mosistsmc180.sp](#) as the transistor model.
3. Write a SPICE deck for NAND3.
4. Run HSPICE using the deck prepared in Step 3. Test all 8 input combinations.
5. Use COSMOS scope to show all input/output combinations.
6. Take a snapshot of the screen showing the waveforms in Step 5.
7. Paste the snapshot taken above in a document. Save this document in PDF format using the name, [nand3wfs.pdf](#).
8. Save the SPICE deck in Plain Text format using the name, [nand3.sp](#).
9. Create a directory named [~/ICD2019/HW2](#) and put the above two files under the directory.
10. Compress the directory use the following command:
[tar cvzf YourID#_HW2.tar.gz HW2](#)
11. Submit your [YourID#_HW2.tar.gz](#) file to ceiba.